



ECSE 323
Digital System Design

Combinational Circuits

Prof. Warren Gross

Material used in this set of slides was based on “*Fundamentals of Digital Logic with VHDL Design*”
by S. Brown and Z. Vranesic

Combinational Circuits


- The values of the outputs of a *combinational circuit* depend only on the values of the signals applied to the inputs
 - (In later chapters we will study circuits whose output depend not only on the values of the input, but also on the past behavior of the circuit....)

Multilevel Synthesis (4.6/4.7)

- We have so far seen two-level realizations of logic functions (assuming the availability of complements at the input)
 - AND stage followed by an OR stage (SOP)
 - OR stage followed by and AND stage (POS)
 - Equivalent NAND-NAND or NOR-NOR networks
- In many technologies, it is not efficient to build the wide gates necessary to implement large functions
 - the “*fan-in*” of the gates available to the designer is not high enough
 - FPGA: array of simple elements that usually have at most 2 - 5 inputs
 - CMOS: Can only put a few transistors in series, say at most 5


Factoring

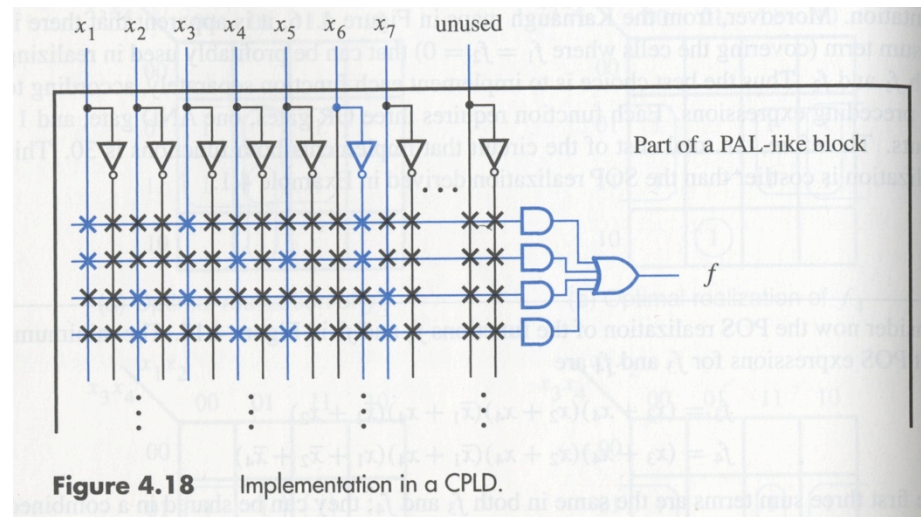Implementation technology dictates strategy



Factoring

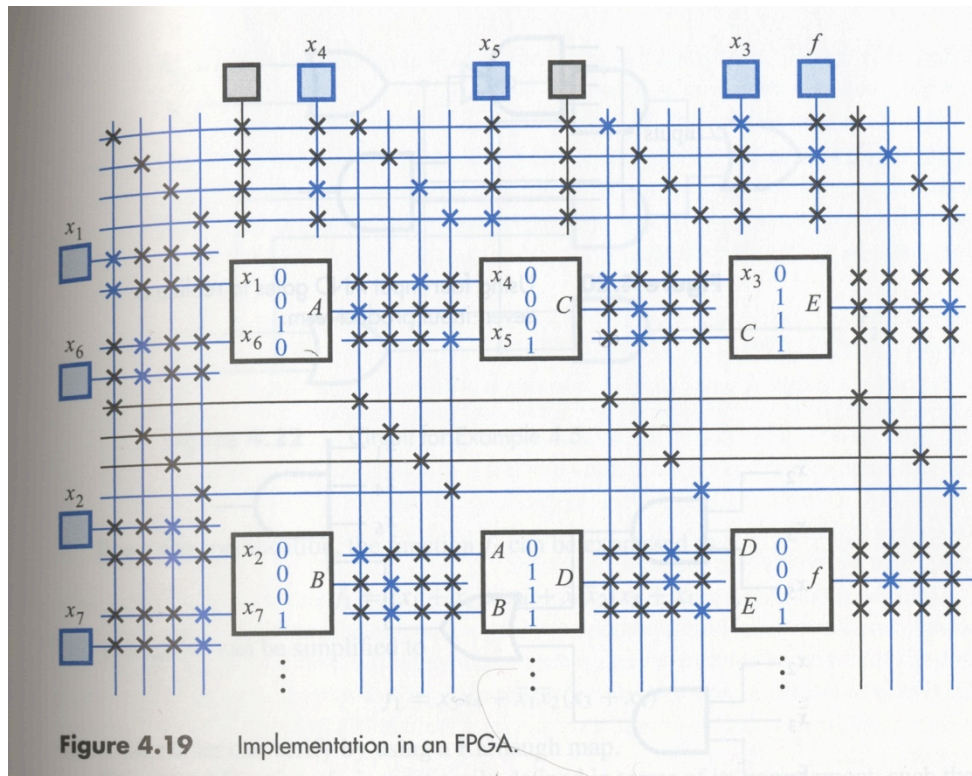Each LUT has a fan-in of 2;
need to factor the
expression accordingly.



```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY func3 IS
    PORT ( x1, x2, x3, x4, x5, x6, x7 : IN    STD_LOGIC ;
          f                               : OUT STD_LOGIC );
END func3 ;

ARCHITECTURE LogicFunc OF func3 IS
BEGIN
    f <= (x1 AND x3 AND NOT x6) OR
        (x1 AND x4 AND x5 AND NOT x6) OR
        (x2 AND x3 AND x7) OR
        (x2 AND x4 AND x5 AND x7) ;
END LogicFunc ;


```

Impact on Wiring Complexity

(same example as previous, fan-in = 4)

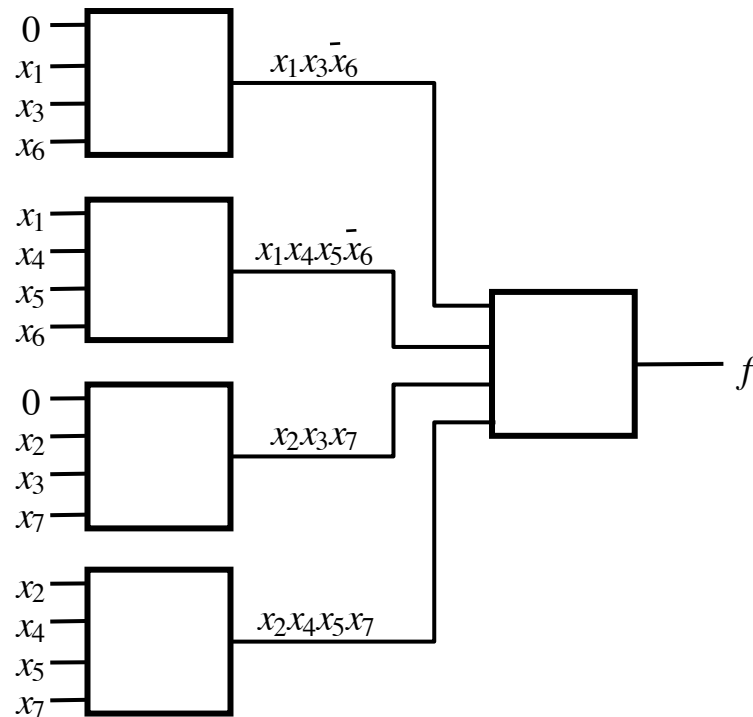


(a) Sum-of-products realization

 

(b) Factored realization

Another Example

 

e.g. Maximum fan-in of 4

See Example 4.5 in the text
for another example of
factorization



Multilevel circuits usually
imply longer propagation
delay

Decomposition

$$f = \bar{x}_1 x_2 x_3 + x_1 \bar{x}_2 x_3 + x_1 x_2 x_4 + \bar{x}_1 \bar{x}_2 x_4$$

Factor common terms...
  
$$f = (\bar{x}_1 x_2 + x_1 \bar{x}_2) x_3 + (x_1 x_2 + \bar{x}_1 \bar{x}_2) x_4$$



Disjoint decomposition

Another Example

$x_3x_4 \backslash x_1x_2$					
		00	01	11	10
00		1			
01			1	1	1
11		1			
10			1	1	1

$$x_5 = 0$$

$x_3x_4 \backslash x_1x_2$					
		00	01	11	10
00					
01		1	1	1	1
11					
10		1	1	1	1

$$x_5 = 1$$

Look for patterns in Karnaugh map
Each pattern only depends on the variables that define columns in each row

e.g. Blue pattern is a subfunction


Another Example

x_3x_4 \ x_1x_2					
		00	01	11	10
00		1			
01		1	1	1	1
11		1			
10		1	1	1	1

$x_5 = 0$

x_3x_4 \ x_1x_2					
		00	01	11	10
00					
01		1	1	1	1
11					
10		1	1	1	1

$x_5 = 1$

 


$$g(x_1, x_2, x_5) = x_1 + x_2 + x_5$$

$$k(x_3, x_4) = x_3'x_4 + x_3x_4'$$


$$f(x_1, x_2, x_3, x_4, x_5) = h[g(x_1, x_2, x_5), k(x_3, x_4)] \\ = kg + k'g'$$

11 gates (including input inverters) and 19 inputs, max fan in = 3
 2-level minimal SOP: 14 gates, 41 inputs, max fan in = 8


Multilevel NAND and NOR Circuits

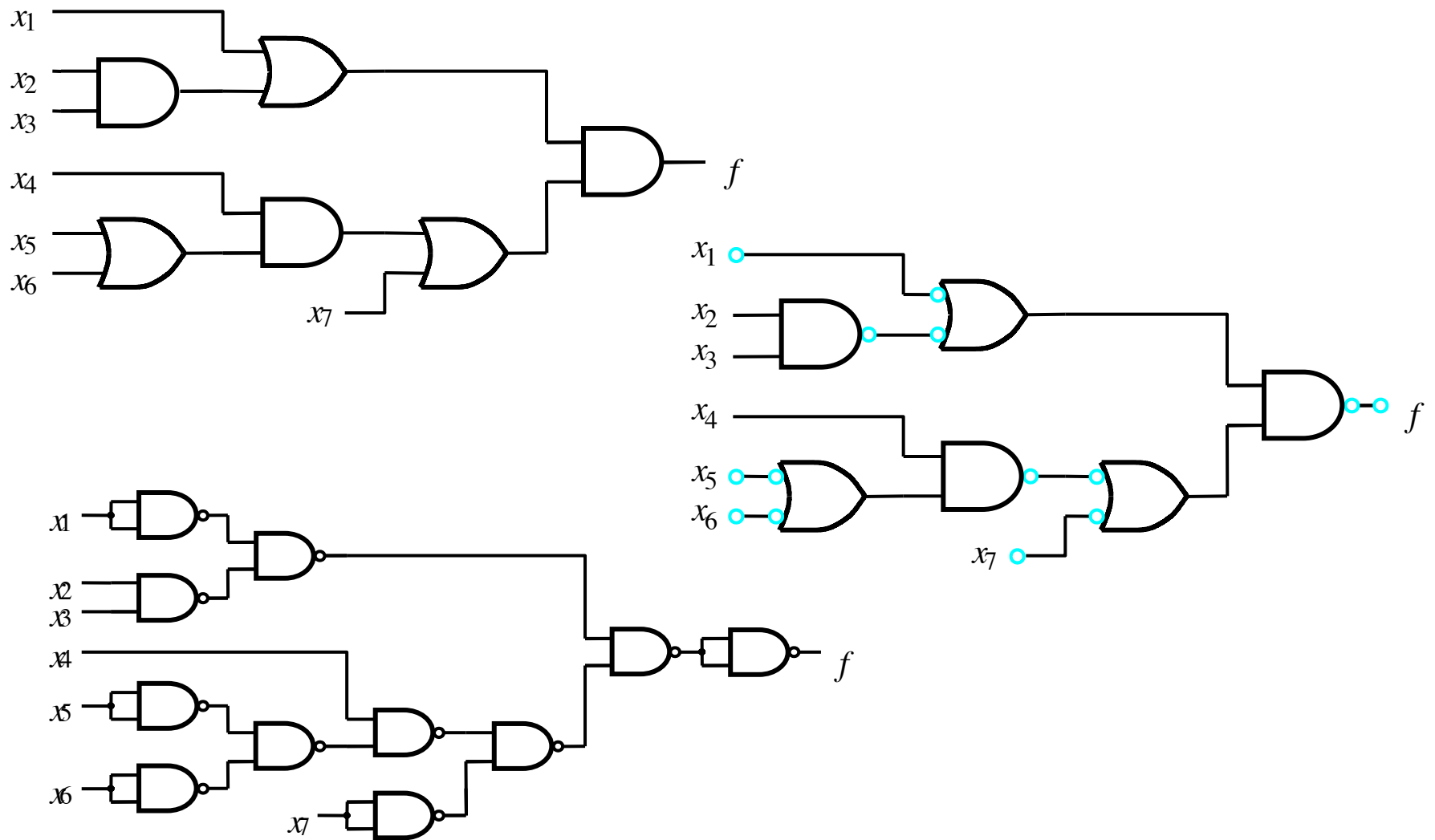

Analysis

 

 
Interpretation of SOP form from NAND-NAND circuit




$$f = \overline{\overline{\overline{x_5(x_4(x_3(x_2 x_1))})}}$$

Successive application of de Morgan yields an unwieldy expression.

 
Expression greatly simplified by concerting selected NAND-NAND to AND-OR



NAND = OR with inputs inverted

 

Substitute

 

Remove redundant inverters


$$f = \bar{x}_5 + (x_4(\bar{x}_3 + (x_1 x_2)))$$

$$f = \bar{x}_5 + \bar{x}_3 x_4 + x_1 x_2 x_4$$

Combinational Circuit Building Blocks

- Chapter 6
- There are a few basic building blocks commonly used to build up larger circuits
 - Multiplexers / Demultiplexers
 - Decoders / Encoders
 - Arithmetic circuits


Multiplexers

 


s	f
0	w_0
1	w_1

(a) Graphical symbol for 2-to-1 MUX

(b) Truth table

 


(c) Sum-of-products circuit

 

(a) Graphic symbol


s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

 


(c) Circuit


4-to-1 multiplexer.

 

 
Using 2-to-1 multiplexers to build a 4-to-1 multiplexer.



A 16-to-1 multiplexer.

 

 (a) A 2x2 crossbar switch: connects any input to any output




(b) Implementation using multiplexers

Synthesis Using MUXs

- E.g. $f = w_1 \text{ xor } w_2$

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 


(a) Implementation using a 4-to-1 multiplexer


w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

w_1	f
0	w_2
1	$\overline{w_2}$


(b) Modified truth table

 

(c) Circuit

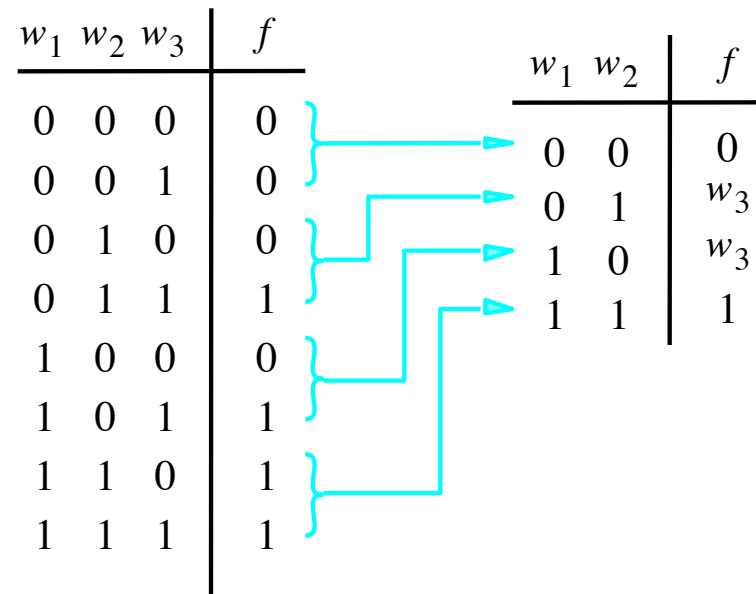

 (a) Modified truth table (can choose any 2 of the 3 input as the select signals)




(b) Circuit

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$w_2 \oplus w_3$

$w_2 \oplus w_3$

(a) Truth table

 


(b) Circuit

- Three-input XOR implemented with 2-to-1 multiplexers.
- Another way to derive the circuit is to write $f = (w_2 \text{ xor } w_3) \text{ xor } w_1$
- Other circuits are possible

w_1	w_2	w_3	f	
0	0	0	0	} w_3
0	0	1	1	
0	1	0	1	} \bar{w}_3
0	1	1	0	
1	0	0	1	} \bar{w}_3
1	0	1	0	
1	1	0	0	} w_3
1	1	1	1	

(a) Truth table

 


(b) Circuit

Three-input XOR function implemented with a 4-to-1 multiplexer.

MUX Synthesis: Shannon's Expansion

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

 

(b) Circuit


(a) Truth table for 3-input majority function

Decompose in terms of variables used for select inputs


Shannon's Expansion Theorem

- Any Boolean Function $f(w_1, \dots, w_n)$ can be written in the form

$$f(w_1, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$


$$f_{\bar{w}_1}$$

Cofactor of f with respect to w_1'


$$f_{w_1}$$

Cofactor of f with respect to w_1

- In general:

- E.g. 3-input majority function

- E.g. 3-input XOR

Expansion in terms of more variables


$$f(w_1, \dots, w_n) = \bar{w}_1 \bar{w}_2 \cdot f(0, 0, w_3, \dots, w_n) + \bar{w}_1 w_2 \cdot f(0, 1, w_3, \dots, w_n) \\ + w_1 \bar{w}_2 \cdot f(1, 0, w_3, \dots, w_n) + w_1 w_2 \cdot f(1, 1, w_3, \dots, w_n)$$

- Implement using a 4-to-1 MUX
 - Expansion in terms of all n variables
- canonical sum-of-products form

 Examples

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$


$$f = \bar{w}_1 \bar{w}_2 (\bar{w}_3) + \bar{w}_1 w_2 (\bar{w}_3) + w_1 \bar{w}_2 (w_3) + w_1 w_2 (1)$$



$$f = w_1 w_2 + w_1 w_3 + w_2 w_3$$


$$f = \bar{w}_1(w_2 w_3) + w_1(w_2 + w_3 + w_2 w_3)$$
 
$$f = \bar{w}_1(w_2 w_3) + w_1(w_2 + w_3)$$



Decoders

 
- Only one output is asserted at a time
 - *one-hot* encoding
 - Output corresponds to one valuation of the inputs
 - $En = 0 \rightarrow$ no outputs asserted




n -to- 2^n binary decoder.

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 


(b) Graphical symbol

 

(c) Logic circuit


Larger decoders can be built by extending this SOP structure or by combining smaller decoders

2-to-4 decoder

 


Top decoder is enabled if $w_2 = 0$ and bottom is enabled if $w_2 = 1$

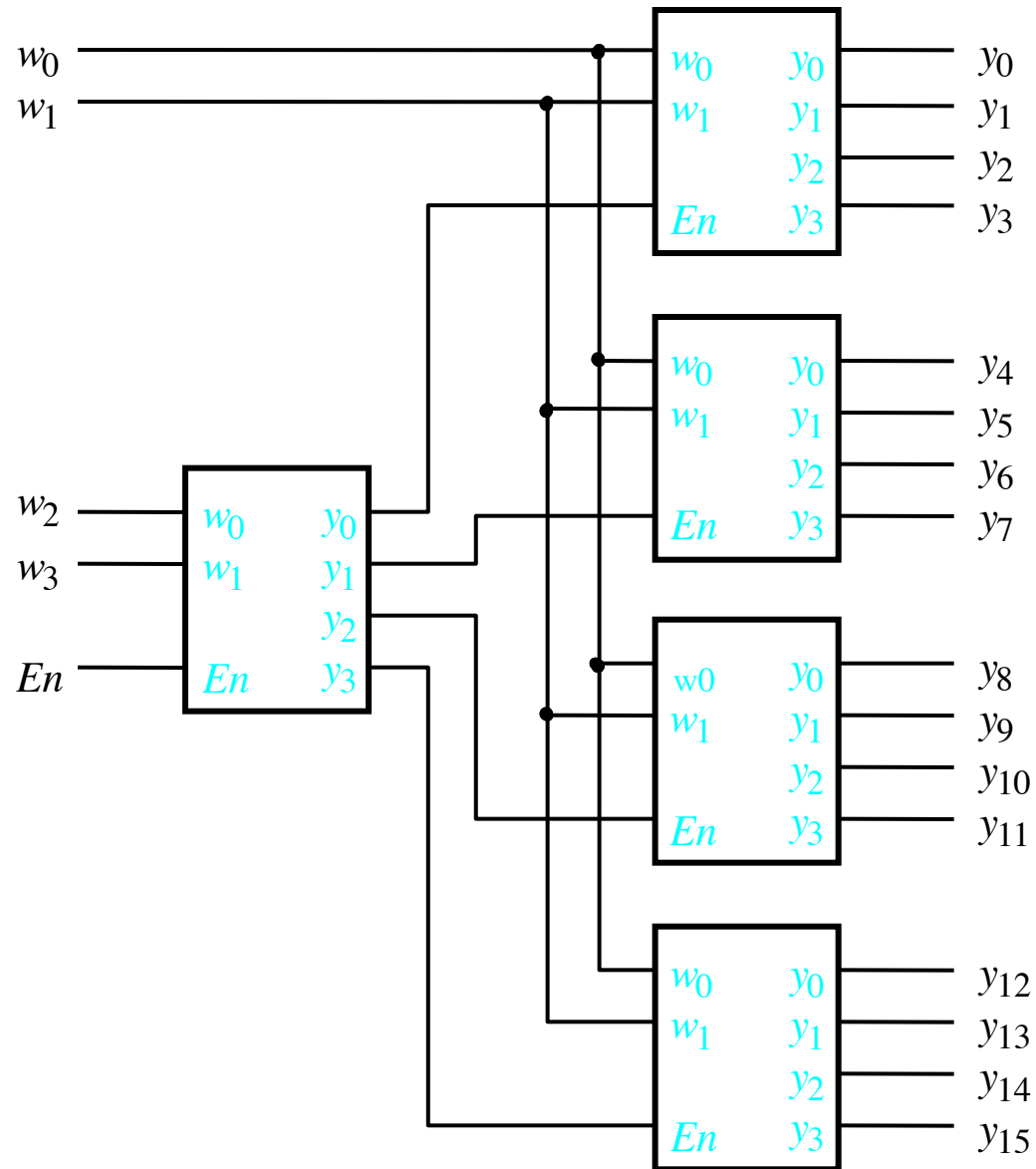A 3-to-8 decoder using two 2-to-4 decoders.



A 4-to-16 decoder built using a decoder tree

Application: MUX

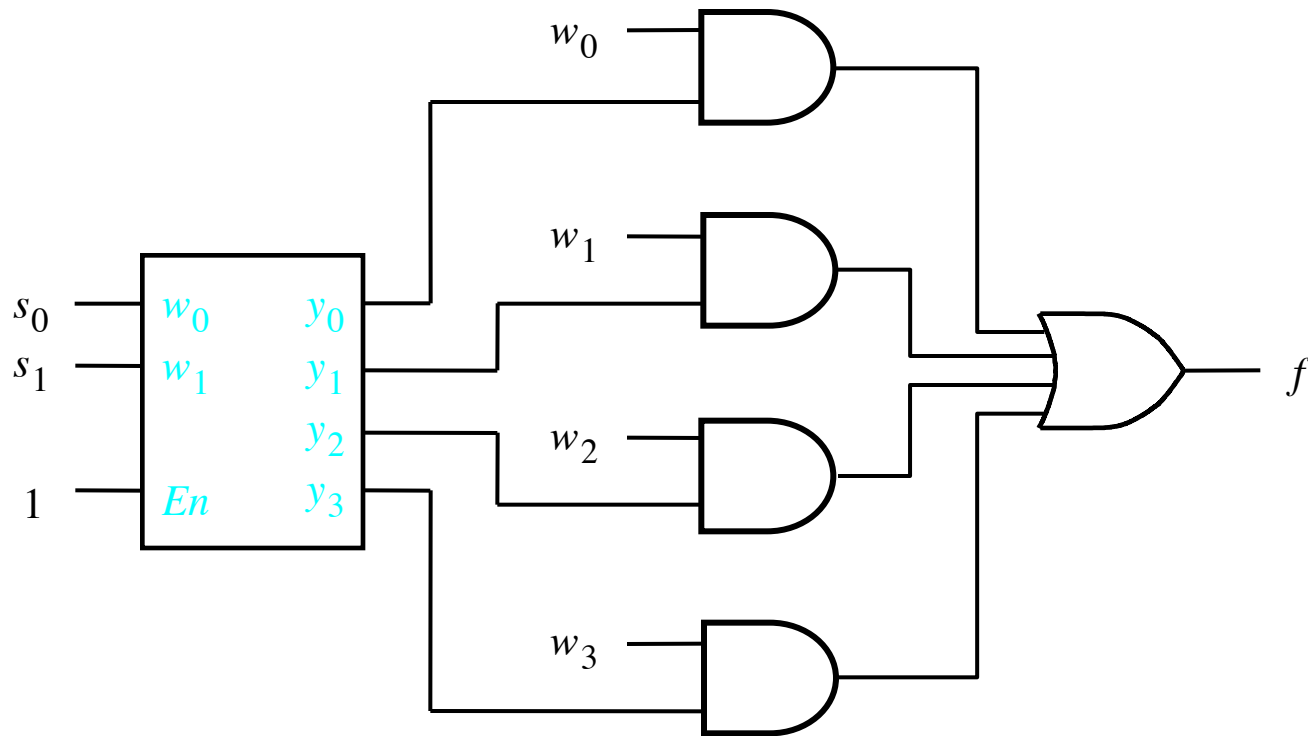


A 4-to-1 multiplexer built using a decoder.


Application: Demultiplexers

- Places the value of a single input onto one of 2^n outputs, controlled by n select bits
 - Can be implemented using a decoder
 - e.g. 2:4 decoder can implement a 1:4 demux using the enable as data input

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

 


Application: Read-Only-Memory

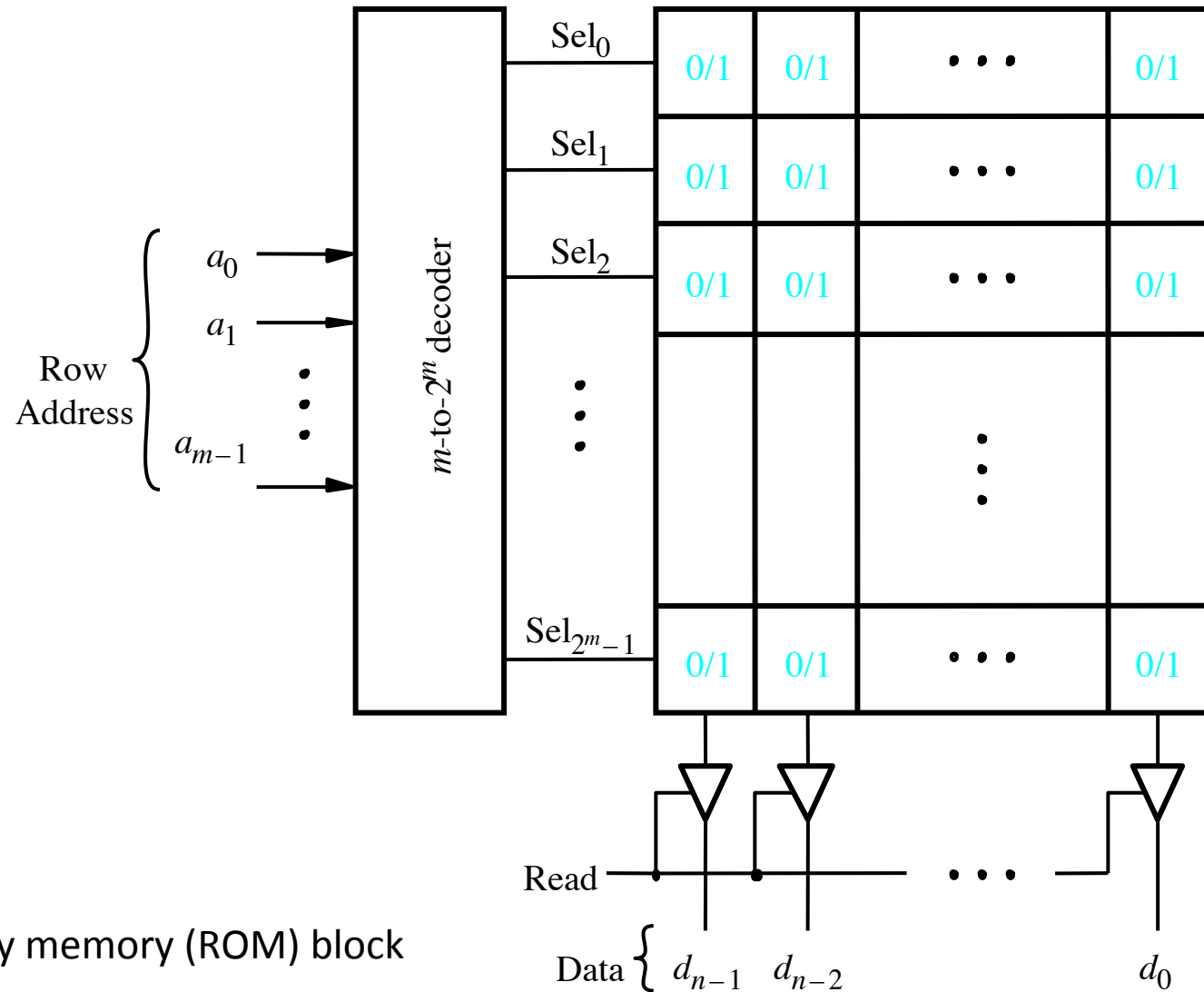

A $2^m \times n$ read-only memory (ROM) block

Encoders

 - Used to compactly represent information
 - Exactly one of the inputs should be 1
 - Output is the binary number that identifies which input is 1



2^n -to- n binary encoder.

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Truth table for 4:2 binary encoder

Priority Encoders

- Output indicates which input of the highest *priority* is active
 - Lower priority inputs are ignored
 - Output z indicates none of the inputs are 1

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1


4-to-2 priority encoder.

w_0 : lowest priority

w_{2^n-1} : highest priority

Arithmetic Building Blocks

 - Comparators
 - Inputs A and B are unsigned n -bit binary numbers
 - E.g.: 4-bit comparator
- Truth table is large even for moderate values of n



$$A = a_3a_2a_1a_0$$

$$B = b_3b_2b_1b_0$$

$$i_k = 1 \text{ if } a_k = b_k$$

Starting at MSB, find first position k for which $a_k \neq b_k$

If $a_k = 0$ and $b_k = 1$ then $A < B$

If $a_k = 1$ and $b_k = 0$ then $A > B$

e.g: A = 0 1 1 0

B = 0 1 0 1

$$AeqB = i_3i_2i_1i_0$$

$$AgtB =$$

$$AltB =$$

Other Arithmetic Circuits

- Adders (and subtractors)
 - Many different adder circuits
- Multipliers / Dividers
 - Build out of multiple adders and subtractors
 - In general can require many logic gates to implement
- Multiply or divide by powers of 2
 - Use a *shifter* circuit
 - Shifter design including VHDL is given in Examples 6.31, 6.32, 6.34 and 6.35

Full Adder (5.2)

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table


$x_i y_i$	00	01	11	10
c_i				
0		1		1
1	1		1	

$$s_i = x_i \oplus y_i \oplus c_i$$

$x_i y_i$	00	01	11	10
c_i				
0			1	
1		1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


(b) Karnaugh maps

 

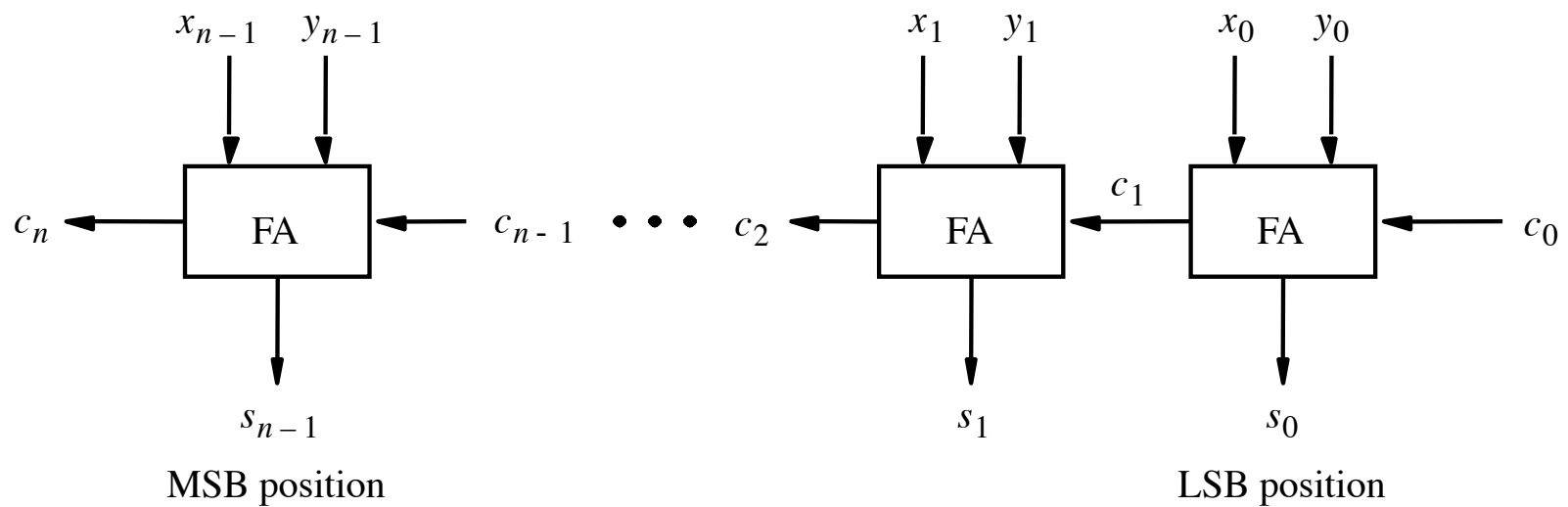(c) Circuit

Ripple Carry Adders


- You have seen binary n -bit ripple carry adders in ECSE 221 (see 5.2.2)
 - The sum is available after a delay of $n\Delta t$ where Δt is the delay of a full-adder



Carry-Lookahead Adder (5.4)

$$\begin{aligned}c_{i+1} &= x_i y_i + x_i c_i + y_i c_i \\&= x_i y_i + (x_i + y_i) c_i \\&= g_i + p_i c_i \\&= g_i + p_i (g_{i-1} + p_{i-1} c_{i-1}) \\&= g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-1} \\&= g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + \cdots + p_i p_{i-1} \cdots p_2 p_1 g_0 + p_i p_{i-1} \cdots p_1 p_0 c_0\end{aligned}$$

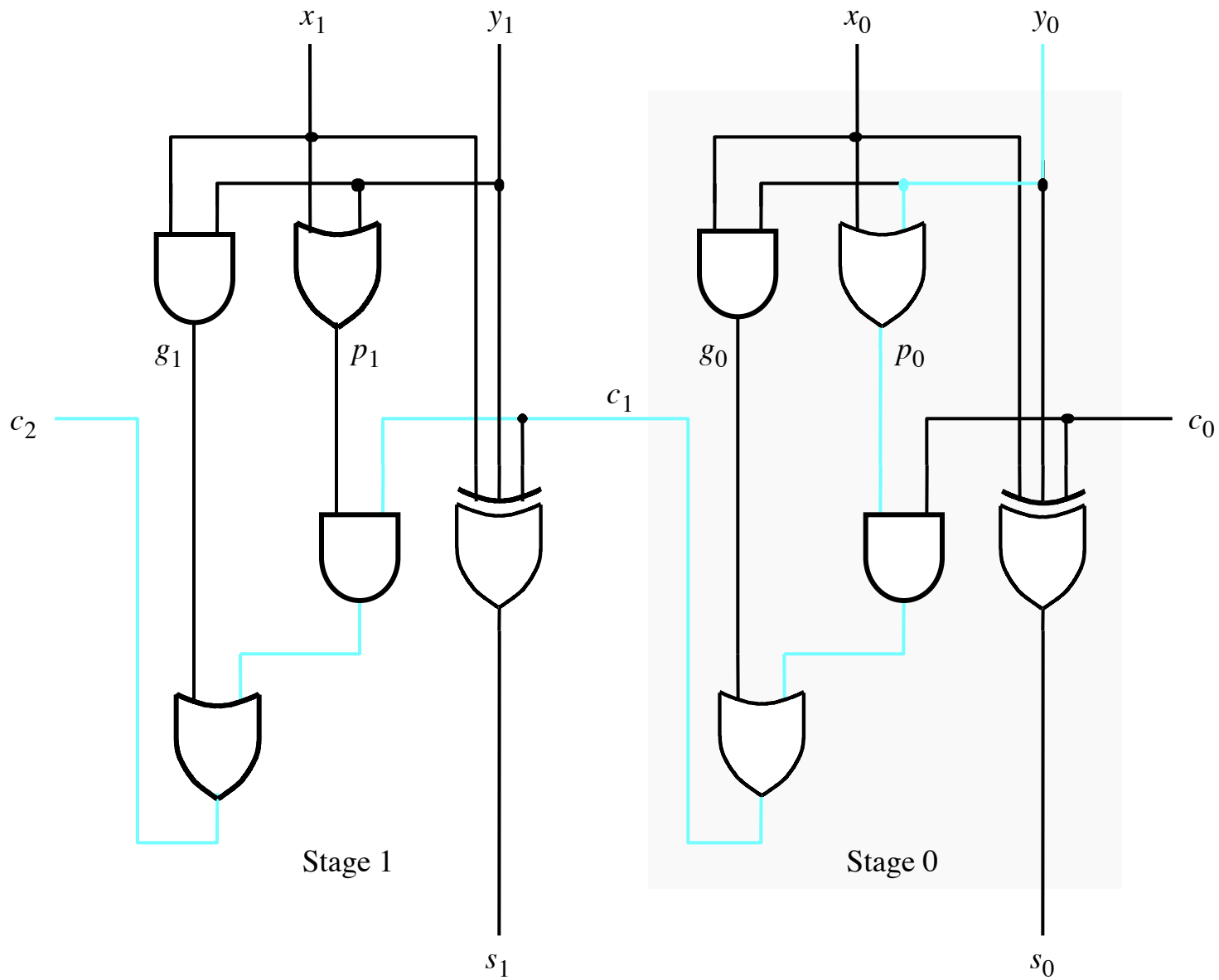
- g_i : **carry generate** = $x_i y_i$
- p_i : **carry propagate** = $x_i + y_i$
 - g_i and p_i are independent of the carry-in c_i
 - The carry-out c_{i+1} is computed with a fast two-level circuit independent of the carry-in



ripple-carry adder

$$\text{Delay} = 2n + 1 \text{ gates}$$

- After the g and p signals settle in 1 gate delay, **all output carries are evaluated simultaneously** in 2 gate delays and then one additional gate delay is needed to get the sum outputs
- Total delay of the entire adder is 4 gate delays total independent of n
- The trade-off is higher circuit complexity as n increases
- *Hierarchical* designs group input bits into blocks implemented with carry-lookahead adders and using ripple carries between blocks
- There are many different fast adder structures
 - Choice of adder structure depends on the constraints (delay, area, power) and the target technology
 - e.g. FPGAs are actually rather good at implementing carry-ripple adders because of dedicated fast carry chain wires

 

Self-Study

- Code-converters (6.4)
- VHDL for combinational circuits (4.12, 5.5, 6.6)
- As usual, the last section in each chapter of the textbook has solved practice problems (4.14, 5.9, 6.8)